

CSC 137 MOCK MIDTERM 1

Show your work clearly to earn points. Work not shown will not earn any points.

Date:

Instructor: Dr. Ilkan Çokgör

Total: 20 points

Student Name:

Student Number:

1) The binary numbers below are in signed 2's compliment representation.

$$01001 + 01000$$

- a) Perform the given binary operation. (1 point)
- b) Is there an overflow condition, and explain why or why not? (2 points)

2) a) Generate the truth table for the following function: (2 points)

$$F = XY + X'Z + YZ$$


- b) Write the Boolean equation of this function in canonical sum-of-products form. (3 points)
- c) Use K-maps to simplify the Boolean equation. (3 points)
- d) Draw the logic diagram of the simplified function using NOT, AND, OR gates. (2 points)

3) Implement the following truth table using an 8:1 multiplexer. (3 points)

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Exam continues on the next page.

 4) In the following diagrams, the signals are connected to a D-latch and a D-Flip Flop as shown. Draw the timing diagrams for the "Q for latch" and the "Q for Flip Flop" outputs. (4 points)



Solutions:

1) The binary numbers below are in signed 2's complement representation.

$$01001 + 01000$$

a) Perform the given binary operation. (1 point)

b) Is there an overflow condition, and explain why or why not? (3 points)

a)

$$\begin{array}{r} 01001 \\ + 01000 \\ \hline 10001 \end{array}$$

b) Yes, there is an overflow condition because adding two positive numbers resulted in a negative number.

2) a) Generate the truth table for the following function: (3 points)


$$F = XY + X'Z + YZ$$

X	Y	Z	XY	X'Z	YZ	F
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	0	1	1	1
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	0	1
1	1	1	1	0	1	1

b) Write the Boolean equation of this function in canonical sum-of-products form. (3 points)


$$F = X'Y'Z + X'YZ + XYZ' + XYZ$$

 c) Use K-maps to simplify the Boolean equation. (3 points)




$$F = X'Z + XY$$

 d) Draw the logic diagram of the simplified function using NOT, AND, OR gates. (2 points)



3) Implement the following truth table using an 8:1 multiplexer. (4 points)

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

4) In the following diagrams, the signals are connected to a D-latch and a D-Flip Flop as shown. Draw the timing diagrams for the "Q for latch" and the "Q for Flip Flop" outputs. (4 points)

