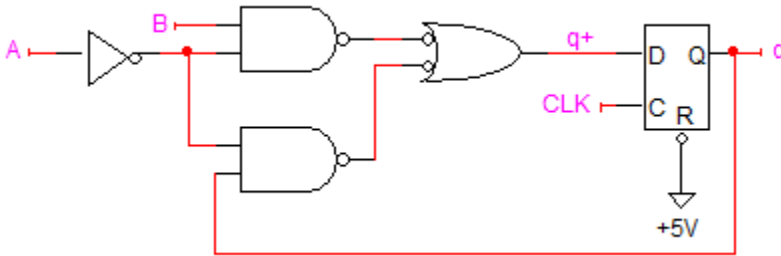


CSC 137 Cokgor Homework 3 (5 points)

Consider the state machine circuit below:



- 1) Write the equation for  $q^+$ . (0.5 point)
- 2) Create the K-map for  $q^+$ . (1 point)
- 3) Create the state transition table using the K-map. (1.5 point)
- 4) Create the state transition diagram and explain the purpose of the circuit. (2 point)