

(Exercises reference: David M. Harris, Sarah L. Harris, Digital Design and Computer Architecture, 2nd Edition, Elsevier, 2013, ISBN-13: 978-0-12-394424-5)

- 1) Given the input waveforms shown in figure below, sketch the output, Q, of an SR latch.



- 2) Given the input waveforms shown in figure below, sketch the output, Q, of a D latch.




- 3) Given the input waveforms shown in figure below, sketch the output, Q, of a D flip-flop.




- 4) The toggle (T) flip-flop has one input, CLK, and one output, Q. On each rising edge of CLK, Q toggles to the complement of its previous value. Draw a schematic for a T flip-flop using a D flip-flop and an inverter.

- 5) Design a synchronously settable D flip-flop using logic gates.

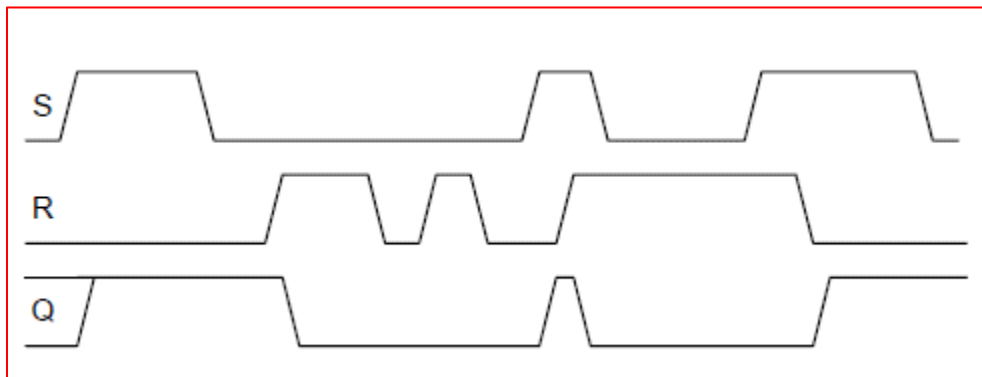
1) Given the input waveforms shown in figure below, sketch the output, Q, of an SR latch.



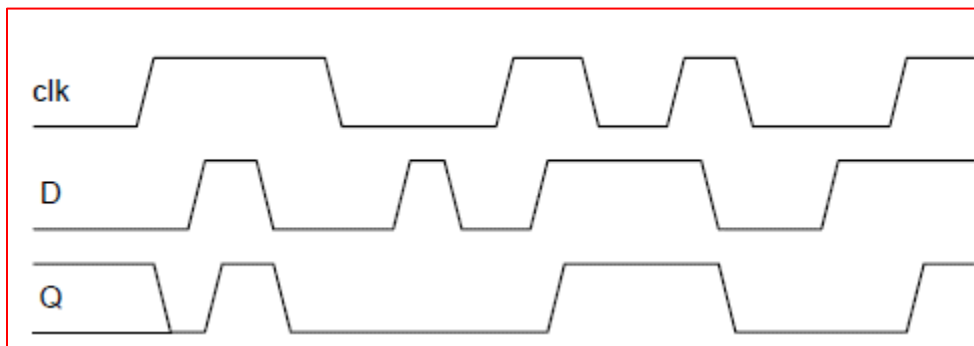
2) Given the input waveforms shown in figure below, sketch the output, Q, of a D latch.



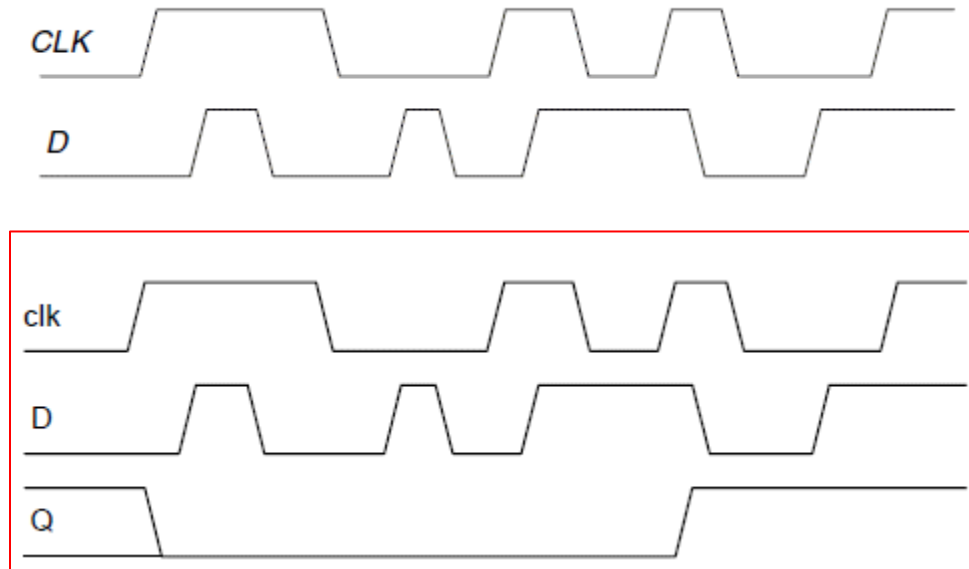3) Given the input waveforms shown in figure below, sketch the output, Q, of a D flip-flop.



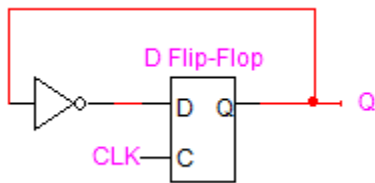4) The toggle (T) flip-flop has one input, CLK, and one output, Q. On each rising edge of CLK, Q toggles to the complement of its previous value. Draw a schematic for a T flip-flop using a D flip-flop and an inverter.



5) Design a synchronously settable D flip-flop using logic gates.

