
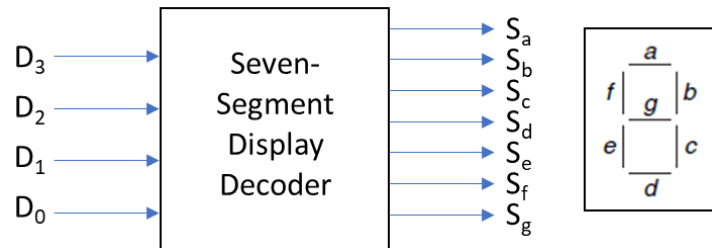


CSC 137 Cokgor Homework 1 (5 points)

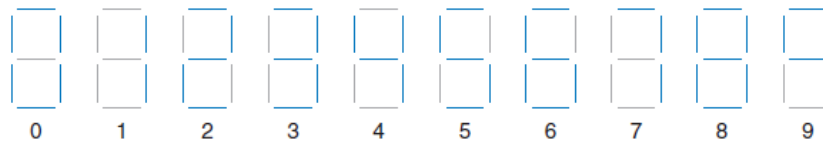A seven-segment display decoder takes a 4-bit data input D_3, D_2, D_1 and D_0 and produces seven outputs to control light-emitting diodes to display a digit from 0 to 9. The seven outputs are often called segments a through g, or S_a-S_g , as shown in the picture below.



See below for how the seven-segment display characters are formed:



The truth table for the outputs are given on page 50 of the Lecture Notes: 'Combinational Logic Small Circuits'. Study the truth tables for the outputs and understand how the inputs, D_0 to D_3 , correspond to the necessary output being 1 based on how the characters are formed in the Figure above.

The K-map and the simplified Boolean equation for S_a is given on page 51 of the lecture notes as an example.

Homework Assignment:

- 1) Use K-maps to derive the Boolean equations for S_b , S_f and S_g . Show your K-map groupings and the Boolean equations clearly in your homework submission. (2 points)
- 2) Implement the logic circuits for S_a , S_b , S_f and S_g in LogicWorks. Submit the screenshot of your LogicWorks circuit in your homework submission. Make sure the circuit is clear and legible. (2 points)
- 3) Simulate your LogicWorks circuit using binary switches on the inputs and binary probes for each output S_a , S_b , S_f and S_g . Set the switches so that you input 3. Take a screenshot of the outputs. Set your switches to input 6. Take a screenshot of the outputs. Set your switches to input 8. Take a screenshot of the outputs. Submit your screenshots. (1 point)